 



Lecture 6

Monday, September 14, 2015 10:01

RS Latch




R	S	
1	1	Hold
0	1	Set
1	0	Clear
0	0	Illegal

 

- illegal input
- "transparent"



change in input immediately changes output

Clocked RS Latch

 



$C=0 \Rightarrow R=S=1$

  $C=1 \Rightarrow S_c = R_c = 0 \Rightarrow \text{Hold}$
 $R_c=1, S_c=0 \Rightarrow \text{Clear}$



D for Data, D Latch
If D is 1, stores 1
D is 0, stores 0

Clocked D Latch

  

C sometimes referred to as enabled



but you want clock edge! shortest time possible

Clock Edges



circuit to detect edges



only detects a rising edge in clock signal


looks similar

but this is shorter

  

Edge Trigger D-Type Flip Flop

now we can build memory circuits.

 

Alternative (Master Slave Flip Flop)

